 




NAND Gates

The block diagram below represents a voting booth monitoring system. For privacy reasons, a voting booth can only be used if the booth on either side is unoccupied. The monitoring system has four inputs and two outputs. Whenever a voting booth is occupied, the corresponding input **Booth A, B, C, or D** is a 1. The first output, **Booth**, is a 1 whenever a voting booth is available. The second output, **Alarm**, is a 1 whenever the privacy rule is violated.



In this activity you will implement NAND only combinational logic circuits for the two outputs **Booth** and **Alarm**. These NAND only designs will be compared with the original AOI implementations in terms of efficiency and gate/IC utilization. In a future activity, these NAND only designs will be compared to the circuits implemented using only **NOR gates**.

Activity

For the sake of time, the truth table and **K-Maps** for the voting booth monitoring systems have been completed for you. Note, for the output **Booth** we took advantage of several **don't care conditions**.

A	B	C	D	Booth	Alarm
0	0	0	0	1	0
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	X	1
0	1	0	0	1	0
0	1	0	1	0	0
0	1	1	0	X	1
0	1	1	1	X	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	X	1
1	1	0	0	X	1
1	1	0	1	X	1
1	1	1	0	X	1
1	1	1	1	X	1

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	1	X	1
$\bar{A}B$	1	0	X	X
AB	X	X	X	X
$A\bar{B}$	1	0	X	0

$$\text{Booth} = \bar{A}\bar{B} + \bar{C}\bar{D}$$

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	0	1	0
$\bar{A}B$	0	0	1	1
AB	1	1	1	1
$A\bar{B}$	0	0	1	0

$$\text{Alarm} = AB + BC + CD$$

1. In your notebook, draw the AOI circuits that implement the simplified logic expressions **Booth** and **Alarm**. Limit this implementation to only 2-input AND gates (74LS08), 2-input OR gates (74LS32), and inverters (74LS04).

Booth – AOI

Alarm – AOI

2. Re-implement these circuits assuming that only 2-input **NAND gates** (74LS00) are available. Draw these circuits in your notebook.

Booth – NAND

Alarm – NAND

3. Using the CDS, enter and test the two logic circuits that you designed. Use switches for the inputs **A**, **B**, **C**, and **D** and a probe or LED circuit for the outputs **Booth** and **Alarm**. Verify that the circuits are working as expected. Print a copy of the circuit and attach it in your notebook. Note: Although the two circuits work independently, they are part of one design and should be simulated, tested, and prototyped together.

Booth and Alarm – CDS

4. Using the DMS, breadboard and test the NAND logic circuits that you designed and simulated. Verify that the circuits are working as expected and the results match the results of the simulation.

Answer the following questions in your engineering notebook:

5. For your AOI implementations, how many ICs (74LS04, 74LS08, and 74LS32 chips) were required to implement your circuits? Note: You're not just counting the number of gates used, but rather, the number of ICs, in whole or part, that were required.
6. For your NAND implementations, how many ICs (74LS00 chips) were required to implement your circuits? Again, we are counting ICs, not gates.
7. In terms of hardware efficiency, how does the NAND implementation compare to the AOI implementation?
8. NAND gates are available with three inputs (74LS10) and four inputs (74LS20). Could either of these chips have been used for this design? If so, how would it have affected the efficiency of the design?